

Solutions to Quiz-1 (Group-B)

IEC102

Q1. Find V_A in the circuit shown in Fig. Q1

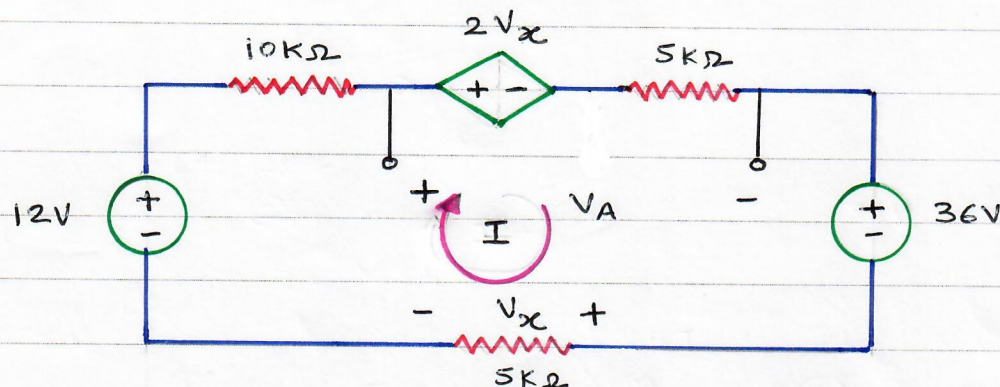


Fig. Q1

Applying KVL around the loop (let I be the loop current)

$$-12 + 10 \times 10^3 I + 2V_x + 5 \times 10^3 I + 36 + V_x = 0$$

$$\Rightarrow 24 + 3V_x + 15 \times 10^3 I = 0 \quad \dots (A)$$

$$\text{But } I = \frac{V_x}{5 \times 10^3}$$

Substituting the value of I in eq (A)

$$\Rightarrow 24 + 3V_x + 15 \times 10^3 \times \frac{V_x}{5 \times 10^3} = 0$$

$$\Rightarrow 24 + 6V_x = 0 \Rightarrow V_x = -4V$$

$$\therefore I = \frac{V_x}{5 \times 10^3} = \frac{-4}{5 \times 10^3} = -0.8 \text{ mA}$$

$$V_A = 2V_x + 5 \times 10^3 I = 2 \times -4 + 5 \times 10^3 \times -0.8 \times 10^{-3}$$

$$= -8 - 4 = -12V$$

$$\boxed{V_A = -12V}$$

$$\therefore I = \frac{-4}{5 \times 10^3} = -0.8 \text{ mA}$$

$$V_A = 2V_x + 5 \times 10^3 I = 2(-4) + 5 \times 10^3 \times -0.8 \times 10^{-3} = -8 - 4 = -12V$$

Find V_1 , V_2 , and V_3 in the circuit of Fig. Q2 using nodal analysis. (Use the concept of supernode).


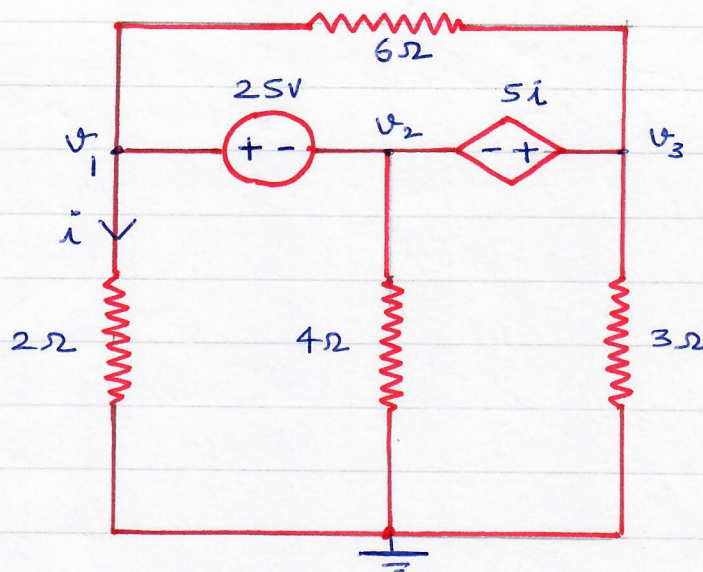


Fig. Q2

Sol.

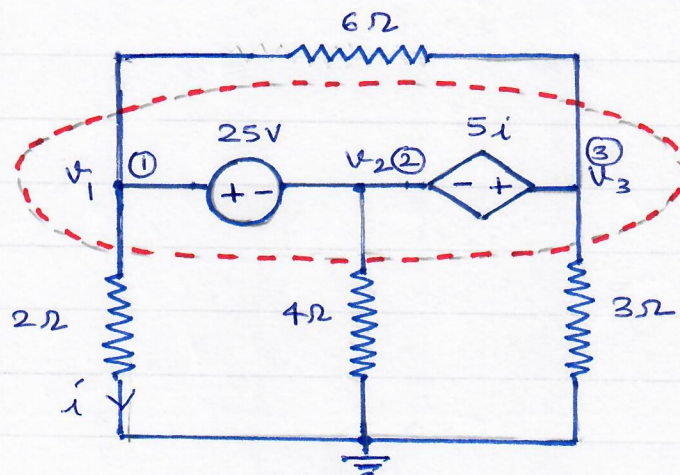

Considering the combination of node ①-②-③ as supernode

Applying KCL at supernode ①-②-③

$$\frac{V_1}{2} + \frac{V_2}{4} + \frac{V_3}{3} + \frac{V_1 - V_3}{6} + \frac{V_3 - V_1}{6} = 0$$

$$\Rightarrow \boxed{6V_1 + 3V_2 + 4V_3 = 0} \dots \text{ (A)}$$

$$\boxed{V_1 - V_2 = 25} \dots \textcircled{B}$$

Since there is an independent voltage source in between them

$$V_3 - V_2 = 5i$$

\therefore there is a dependent ^{voltage} source ($5i$) in between then.

but $i = \frac{V_1}{2}$

$$\therefore V_3 - V_2 = \frac{5V_1}{2}$$

$$\Rightarrow \boxed{5V_1 + 2V_2 - 2V_3 = 0} \dots \textcircled{C}$$

Writing eqns \textcircled{A} , \textcircled{B} , and \textcircled{C} in matrix form

$$\underbrace{\begin{bmatrix} 6 & 3 & 4 \\ 1 & -1 & 0 \\ 5 & 2 & -2 \end{bmatrix}}_A \underbrace{\begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}}_V = \underbrace{\begin{bmatrix} 0 \\ 25 \\ 0 \end{bmatrix}}_B$$

$$V = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = (A^{-1})B$$

$$\therefore V_1 = 7.608 \text{ V}; V_2 = -17.39 \text{ V}; V_3 = 1.6305 \text{ V}$$

Q3 Use mesh analysis to find the currents i_1 , i_2 , and i_3 in the circuit shown in Fig. Q3

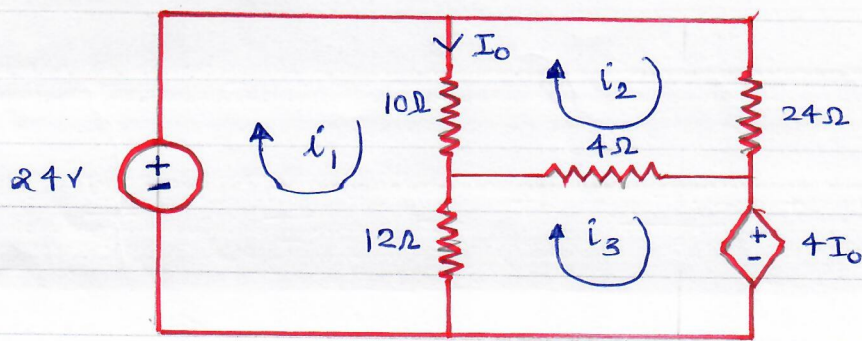


Fig. Q3

Sol. Writing mesh equations around each loop

Loop ①

$$-24 + 10(i_1 - i_2) + 12(i_1 - i_3) = 0$$

$$\Rightarrow 22i_1 - 10i_2 - 12i_3 = 24$$

$$\Rightarrow \boxed{11i_1 - 5i_2 - 6i_3 = 12} \dots \textcircled{A}$$

Loop ②

$$10(i_2 - i_1) + 24i_2 + 4(i_2 - i_3) = 0$$

$$\Rightarrow -10i_1 + 38i_2 - 4i_3 = 0$$

$$\Rightarrow \boxed{-5i_1 + 19i_2 - 2i_3 = 0} \dots \textcircled{B}$$

Loop ③

$$12(i_3 - i_1) + 4(i_3 - i_2) + 4I_0 = 0$$

$$\text{but } I_0 = i_1 - i_2$$

$$\therefore 12(i_3 - i_1) + 4(i_3 - i_2) + 4(i_1 - i_2) = 0$$

$$\Rightarrow -8i_1 - 8i_2 + 16i_3 = 0$$

$$\Rightarrow \boxed{-i_1 - i_2 + 2i_3 = 0} \dots \textcircled{C}$$

Solving ①, ②, and ③

$$i_1 = 2.25 \text{ A}$$

Q4 Use superposition to find V_x in the circuit shown in Fig. Q4

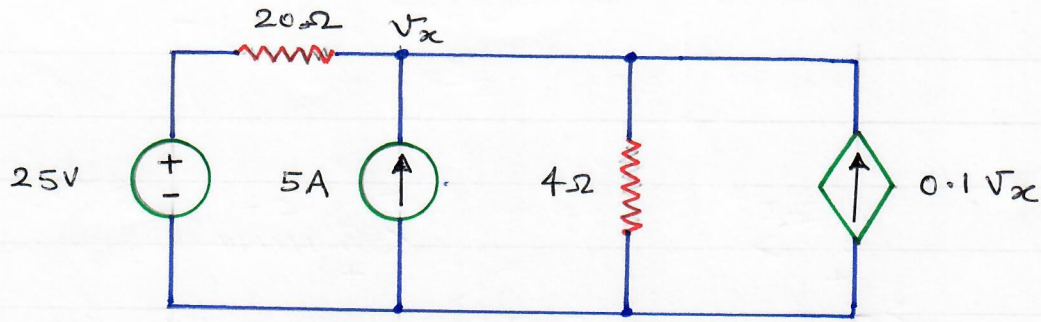


Fig. Q4


Sol.

Taking bottom node as reference node

Let V_x' be the voltage due to 25V voltage source acting alone and V_x'' be the voltage due to 5A current source acting alone

Then using superposition principle $V_x = V_x' + V_x''$

V_x' (due to 25V voltage source)

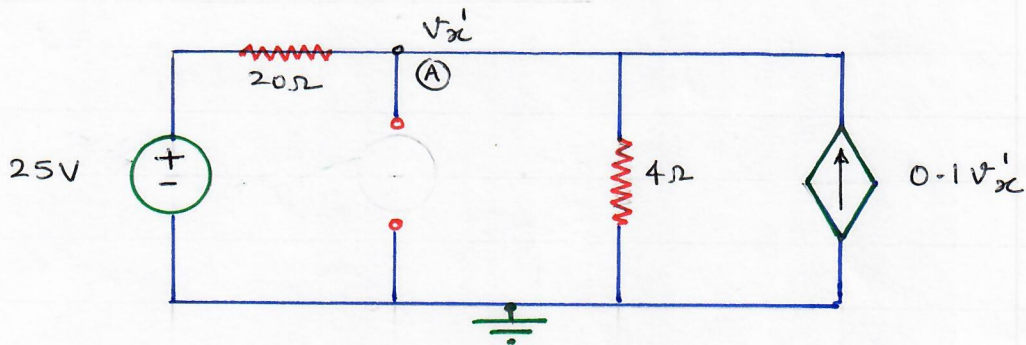

Applying KCL at node (A)


$$\frac{V_x' - 25}{20} + \frac{V_x'}{4} + 0.1V_x' = 0$$

$$\Rightarrow (0.05 + 0.25 + 0.1)V_x' = 1.25$$

$$\Rightarrow 0.4V_x' = 1.25$$

$$\Rightarrow V_x' = 3.125V$$

V_x'' (due to 5A current source)

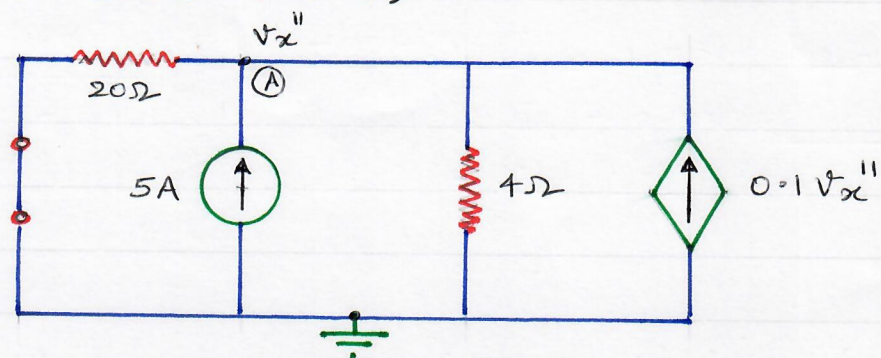

Applying KCL at node (A)

$$\frac{V_x''}{20} - 5 + \frac{V_x''}{4} - 0.1V_x'' = 0$$

$$\Rightarrow (0.05 + 0.25 - 0.1)V_x'' = 5$$

$$\Rightarrow 0.2V_x'' = 5$$

$$\Rightarrow V_x'' = 25$$

When both the sources are active, the voltage V_x at node (A) is

$$V_x = V_x' + V_x''$$

$$= 6.25 + 25$$

$$\Rightarrow V_x = 31.25 \text{ V}$$